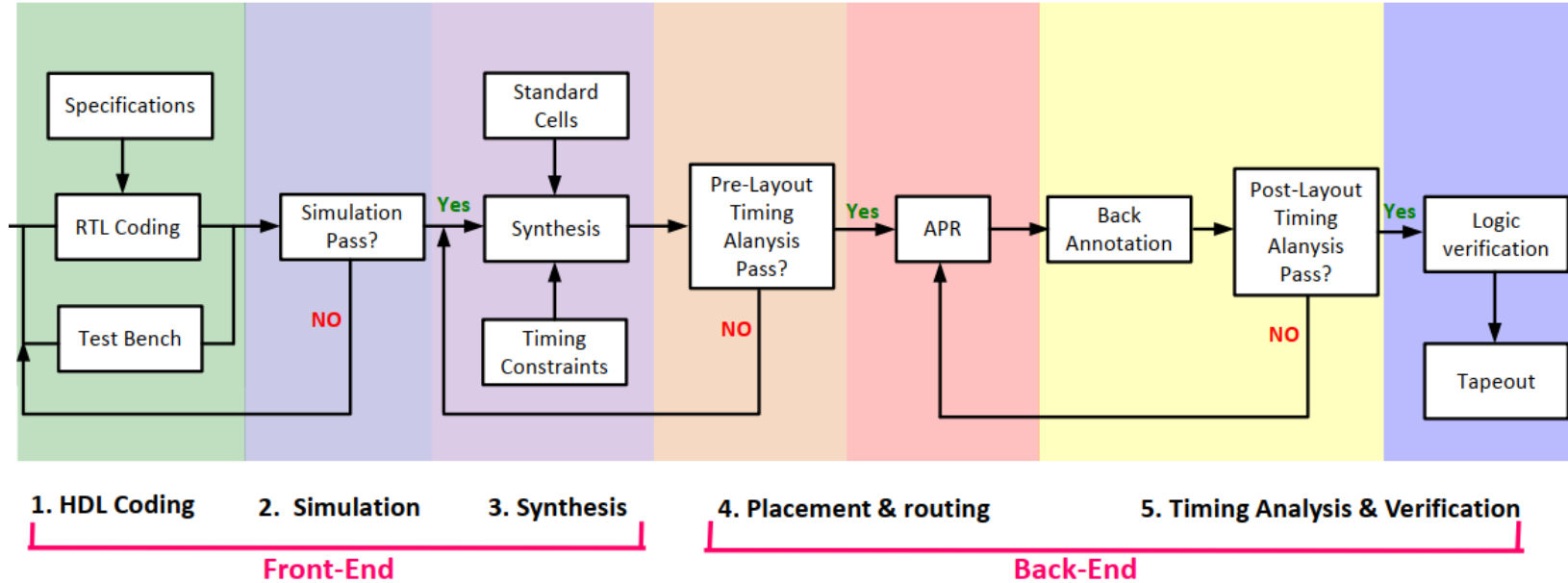


# Chapter 7: ASIC/FPGA Chip Design

## Verilog for Synthesis

Assoc. Prof. Truong Ngoc Son


# ASIC / FPGA Design Flow



# Synthesis

## Synthesis

---

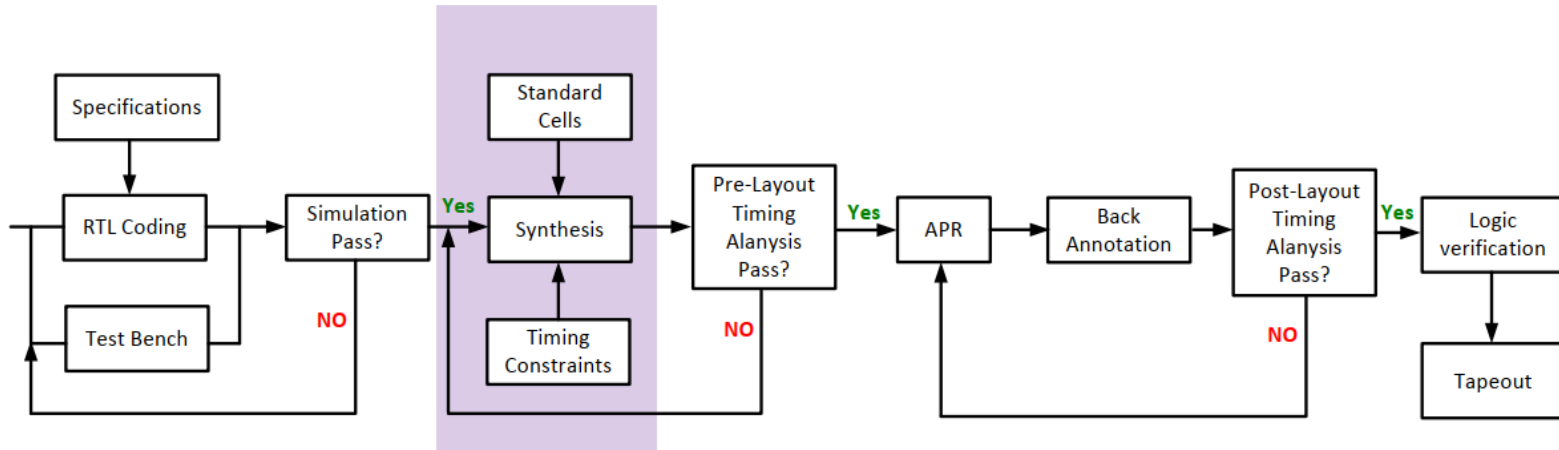

### ❑ Synthesis tool:

- Analyzes a piece of Verilog code and converts it into optimized logic gates
- This conversion is done according to the **“language semantics”**
- ➡ We have to learn these language semantics, i.e., Verilog code.

# Synthesis

## ❑ Why using synthesis tools?

- It is an important tool to improve designers' productivity to meet today's design complexity.
- If a designer can design 150 gates a day, it will take 6666 man's day to design a 1-million gate design, or almost 2 years for 10 designers! This is assuming a linear grow of complexity when design get bigger.

# Synthesis in Different Levels

- ❑ Synthesis can be done in different levels:
  - High-level Synthesis
    - To convert an algorithm-level description to an RTL code
  - RTL Synthesis
    - To convert an RTL code to a gate-level netlist
  - Logic Synthesis
    - To convert the gate-level description to a specific logic library

# Synthesis

## ❑ Synthesis tool: (RTL & Logic Synthesis)

### ➤ Input:

- HDL Code
- “Technology library” file ➡ Standard cells (known by transistor size, 90nm)
  - Basic gates (AND, OR, NOR, ...)
  - Macro cells (Adders, Muxes, Memory, Flip-flops, ...)
- Constraint file (Timing, area, power, loading requirement, optimization Alg.)

### ➤ Output:


- A gate-level “Netlist” of the design
- Timing files (.sdf)

This process is done using various optimization algorithms
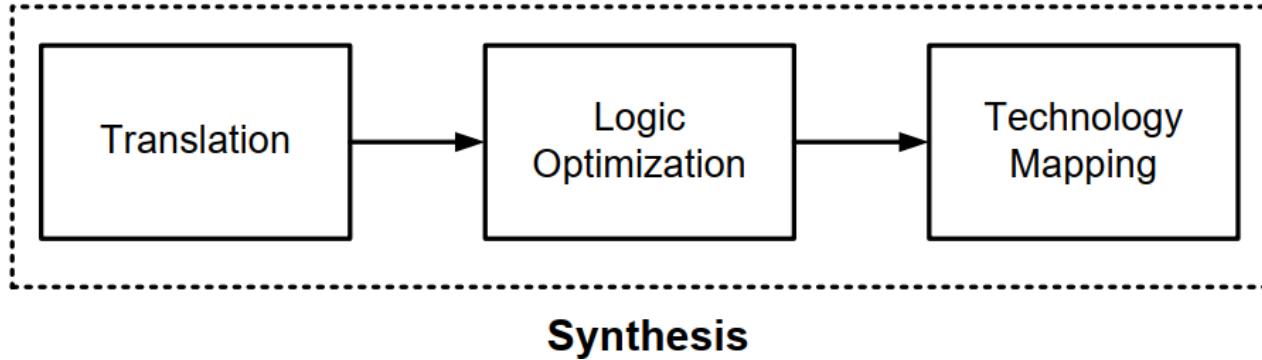
# Synthesis


❑ **Synthesis** = Translation + Logic Optimization + Technology Mapping

- **Translation:** going from RTL to Boolean function
- **Logic Optimization :** Optimizing and minimizing Boolean function
- **Technology Mapping (TM):** Map the Boolean function to the target library


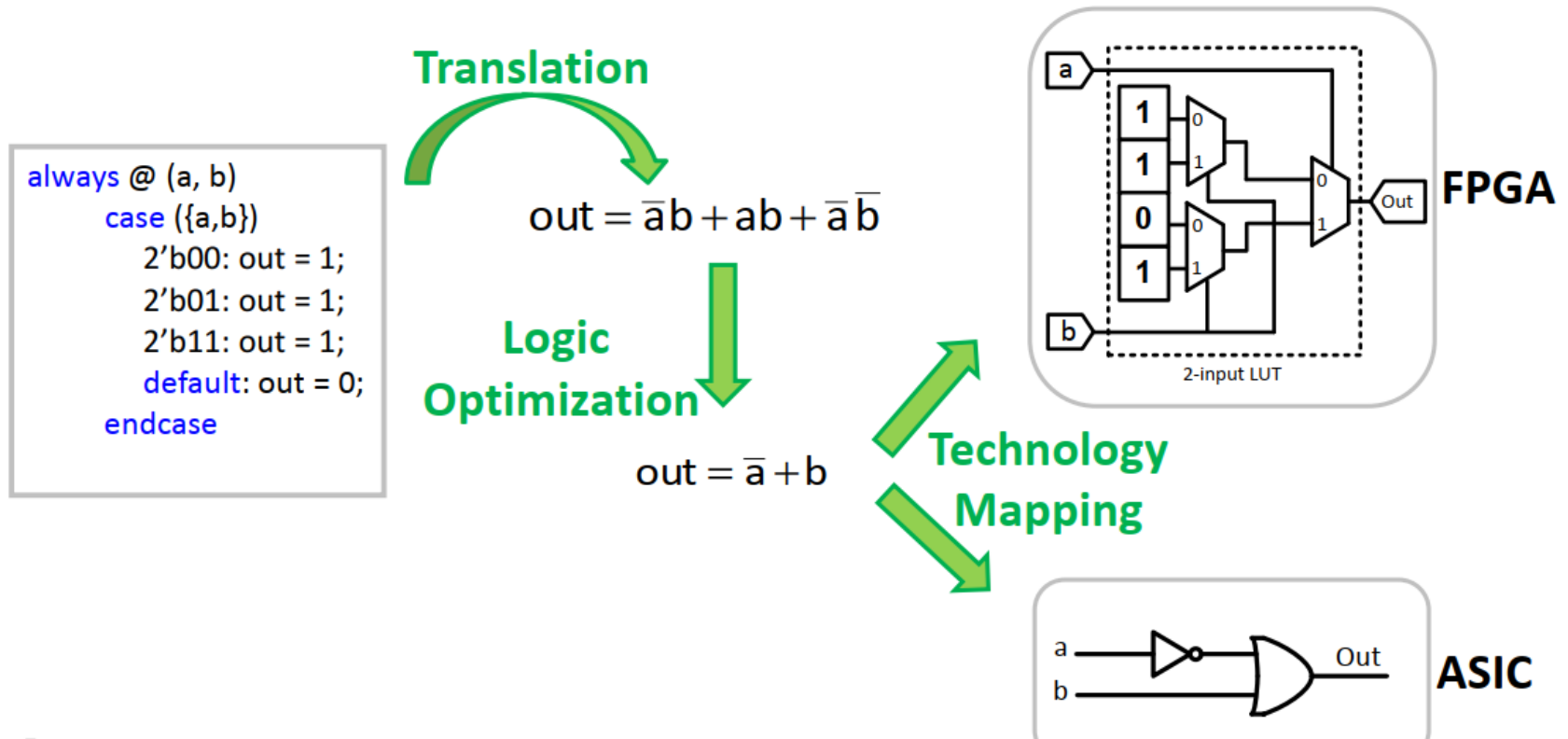
# Synthesis


❑ **Synthesis** = Translation + Logic Optimization + Technology Mapping





# Synthesis Tools

❏ Synthesis tool:

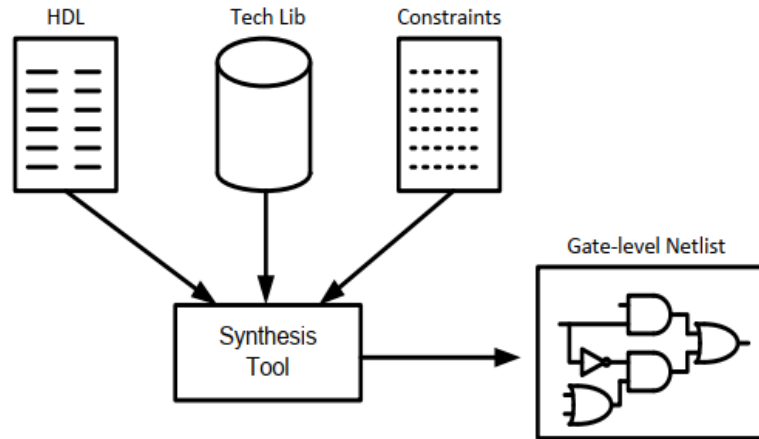


❖ **Example:** A 2-to-1 Multiplexer (2x1-MUX)


```
if (s==0)
  f = a;
else
  f = b;
```

Verilog code  
(has to comply with certain structures)

➡  
**Synthesis  
Tool**

 

Synthesized gate-level

 


Schematic

# Synthesis

```
residue = 16'h0000;  
if (high_bits == 2'b10)  
    residue = state_table[index];  
else  
    state_table[index] = 16'h0000;
```


**HDL Source**

Translate (read)

 

**Generic Boolean  
(GTECH)**

Optimize + Map  
(compile)

 

**Target Technology**

# Synthesis is Constraint-Driven

- ❑ The designer guides the synthesis tool by providing **design constraints**:
  - Timing requirements (max. expected clock frequency)
  - Area requirements
  - Maximum power consumption
- ❑ The synthesis tool uses this information and tries to generate the smallest possible design that will satisfy the timing requirements
- ❑ Without any constraints specified, the synthesis tool will generate a non-optimal netlist, which might not satisfy the designer's requirements


# Synthesis Tools

## ❑ Commercial Synthesis Tools:

Vendor Name	Product Name	Platform
Altera	Quartus II	FPGA
Xilinx	ISE	FPGA
Mentor Graphics	Modelsim, Precision	FPGA/ASIC
Synopsys	Design Compiler	ASIC
Synplicity	Synplify	ASIC
Cadence	Ambit	ASIC
 
# Divide and Conquer for Optimal Synthesis

- ❑ To achieve the best synthesis result, the design is better to be partitioned into smaller parts.
- ❑ **Partitioning:** the process of dividing complex designs into smaller parts
- ❑ Ideally, all partitions would be planned prior to writing any HDL:
  - Initial partitions are defined by the HDL
  - Initial partitions can be modified using Synthesis Tool



# Partitioning

❑ Partition a design into different modules based on the functionality

➤ Pros:

- Separation of the cores that have different functionality
- More manageability of smaller modules
- Easier managements of a design implementation by a team
- Focus to write optimized HDL code for each module
- Possibility of reusing smaller IPs/Block in other designs

➤ Cons:


- Routing congestion or increased die size due to more signaling b/w modules

❑ Not too small not too large modules (~10Kgates)
 
# Partitioning in Verilog


- ❑ **module** statement defines hierarchical blocks (partitions):
  - Instantiation of an entity or module creates a new level of hierarchy
- ❑ Inference of Arithmetic Circuits (+, -, \*) can create a new level of hierarchy
- ❑ Always statements do not create hierarchy

```
module ADR_BLK (...  
  DEC U1 (ADR, CLK, INST);  
  OK  U2 (ADR, CLK, AS, OK);  
endmodule;
```


 
# Good Partitioning (Partition at Register Boundaries)


- ❑ Try to design so the hierarchy boundaries follow register outputs.
- ❑ Related combinational logics in the middle are merged into the same block
  - Combinational optimization techniques can still be fully exploited





 
# Poor Partitioning (Partition at Combinational Logic)

- ❑ Try not to break the Comb. Logics into several hierarchies
- ❑ Synthesis tool must preserve port definitions
- ❑ Logic optimization does not cross block boundaries
  - Adjacent blocks of combinational logic cannot be merged
- ❑ Path from REG A to REG C may be larger and slower than necessary!




# Good Partitioning (Avoid Glue Logic)

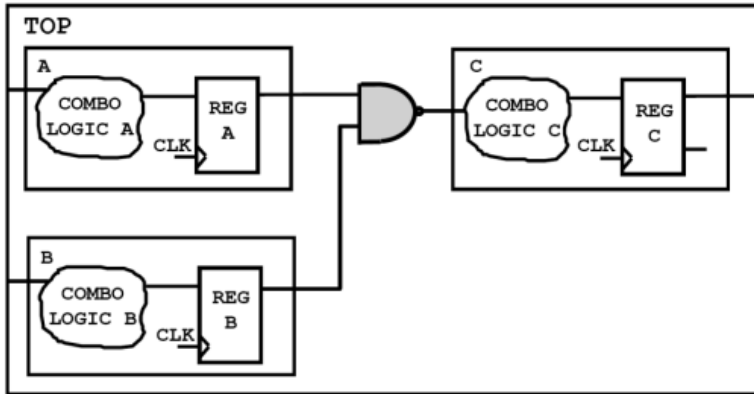

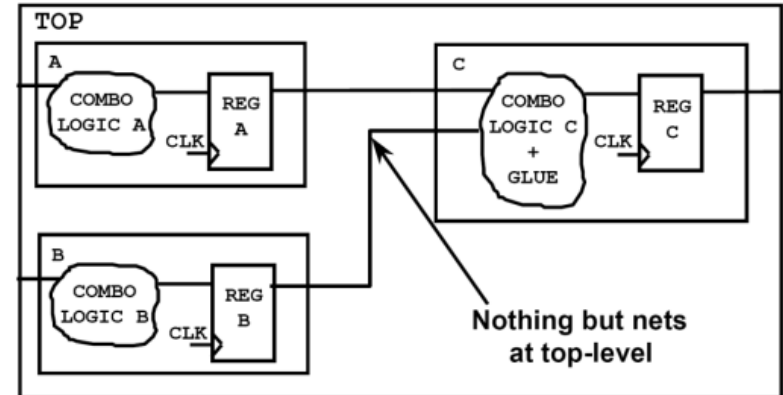**Poor Partitioning**

- ☐ The NAND gate at the top-level serves only to “glue” the instantiated cells.
- ☐ Optimization is limited because the glue logic cannot be “absorbed”
- ☐ Additional compile needed at top-level



**Good Partitioning**

- ☐ The glue logic can now be optimized with other logic
- ☐ Top-level design is only a structural netlist, it does not need to be compiled

# HDL for Synthesis


❑ “Bad” HDL code does not allow efficient optimization during synthesis

➤ Garbage in, garbage out!


❑ Logic synthesizer doesn’t do magic! designer has to take some responsibility in coding.

❖ Example:
 
```
input sub;  
input [3:0] a,b;  
output [3:0] y;  
assign y = sub ? (a-b) : (a+b)
```


 
```
input sub;  
input [3:0] a,b;  
output [3:0] y;  
wire [3:0] tmp;  
assign tmp = sub ? ~b : b;  
assign y = a + tmp + {3'b0,sub}
```



**More efficient**

# HDL for Synthesis (General Guidelines)


## □ Think Hardware:

- Write HDL hardware descriptions
  - Think of the *topology* implied by the code
- Do not write HDL simulation models
  - No explicit delays
  - No file I/O

## □ Think RTL:

- Writing in an RTL coding style means describing:
  - Register architecture
  - Circuit topology
  - Functionality between registers
- Synthesis tool optimizes logic between registers:
  - It does not optimize the register placement

# HDL for Synthesis (General Guidelines)

 

# Synthesizable Constructs

- ❑ Not all Verilog constructs are synthesizable because:
  - Does not make sense in hardware (e.g. \$display, initial block )
  - Not possible to achieve (e.g. delay control like #10)
  - Not support by design flow (e.g. use of tran in P&R)
  - Too difficult or too abstract for the synthesis software (e.g. A / B)

## Synthesizable Constructs

- Ports (input, output, inout)
- Parameter
- module
- wire, reg, tri
- function, task
- always, if, else, case
- assign
- for, while


# Non-Synthesizable Constructs

## Non-Synthesizable Constructs

- Initial (used only in testbenches)
- real (real type data type)
- time (time data type)
- assign for **reg** data types
- comparison to X and Z are ignored (e.g., `a == 1'bz`)
- delays “#” are ignored by synthesis tools as if it is not there

 
# Design for Synthesis (No Timing Loop)

- ❑ Do not use timing loops in the circuit
- ❑ **Timing loop:** when an output of a combinational logic loops back to its input
  - Results in oscillation
  - Complicated timing analysis
  - Timing glitches
- ❑ **Solution:** Add a flip-flop on the feedback path



```
always @ (*)  
  Out = (In1 & Out) | In2;
```

 Oscillates with  $f=1/(T_1+T_2)$   
(Not desired)



```
always @ (posedge gated)  
  Out <= (In1 & Out) | In2;
```

No Oscillation (Desired)




# Latch Inference in Combinational Logic

- ❑ When realizing combinational logic with always block using **if-else** or **case** constructs care has to be taken to avoid latch inference after synthesis
- ❑ The latch is inferred when “incomplete” **if-else** or **case** statements are declared
- ❑ This latch is “unwanted” as the logic is combinational not sequential
- ❑ To avoid latch inference make sure to specify all possible cases “explicitly”
- ❑ Two practical approaches to avoid latch inference:
  - **For if-else construct:**
    1. Initialize the variable before the **if-else** construct
    2. Use else to explicitly list all possible cases
  - **For case constructs:**
    1. Use **default** to make sure no case is missed!
- ❑ If there is some logic path through the always block that does not assign a value to the output a latch is inferred
- ❑ Do **NOT** let it up to the synthesis tool to act in unspecified cases and do specify all cases explicitly.
 
# Avoid Latch Inference in If-else Statements

❖ Example:

```
module DUT (A, B, S, out);  
input A, B, S;  
output reg out;  
always @(*)  
begin  
    if (S==1)  
        out = A;  
end  
endmodule
```




**Latch Inference**

1


2

```
module DUT (A, B, S, out);  
input A, B, S;  
output reg out;  
always @(*)  
begin  
    out = B;  
    if (S==1)  
        out = A;  
end  
endmodule
```
 
```
module DUT (A, B, S, out);  
input A, B, S;  
output reg out;  
always @(*)  
begin  
    if (S==1)  
        out = A;  
    else  
        out = B;  
end  
endmodule
```



**No Latch**

 

**No Latch**


# Avoid Latch Inference in Case Statements

❖ Example:


```
module DUT (A, B, S, out);  
input A, B;  
Input [1:0] S;  
output reg out;  
  
always @(A, B, S)  
begin  
    case (S)  
        2'b00: out = A;  
        2'b01: out = B;  
    endcase  
end  
endmodule
```


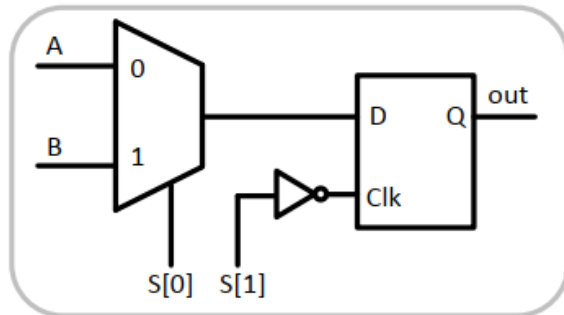
```
module DUT (A, B, S, out);  
input A, B;  
Input [1:0] S;  
output reg out;  
always @(A, B, S)  
begin  
    case (S)  
        2'b00: out = A;  
        2'b01: out = B;  
        default: out = 1'b0;  
    endcase  
end  
endmodule
```



**Latch Inference**

 

**No Latch**

# Clock


- ❑ Clock is the most important signal in the design (golden)
- ❑ Why is it different from other signals?
  - It is a global signal, i.e., it is routed across all modules in the design
- ❑ Treat clock as a golden signal
  - No buffering should be done on clock during coding and synthesis
    - Clock buffering to fix the clock skew is done during clock tree synthesis (part of APR in ASIC flow, which is done automatically)
  - No “clock gating”:
    - Clock should be directly connected to flip-flops without any logic gating
    - Otherwise, it results in clock skew in the design (undesired!)

# Clock (No Internally Generated Clock)

- ❑ Do not use internally generated clocks

```
always @ (posedge Clk)
    Out1 <= In1;

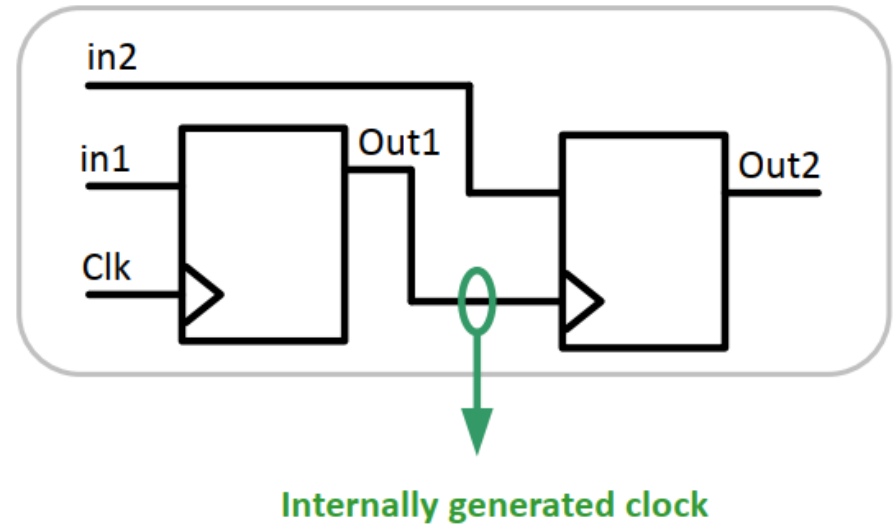always @ (posedge Out1)
    Out2 <= In2;
```



- ❑ Complicates the timing analysis
  - Setup time
  - Hold time
- ❑ Difficult to deal with during synthesis


# Clock (No Gating)

## Clock (No Gating)

---


- ❑ **Gated clock:** clock that is enabled by an enable signal
- ❑ Applications:
  - Used for power saving to switch off part of the chip in fraction of time
- ❑ Avoid clock gating as much as possible
  - Because results in clock skew
  - Not a golden signal anymore!
 
```
assign gated = Clk & Enable  
  
always @ (posedge gated)  
    Out <= In;
```


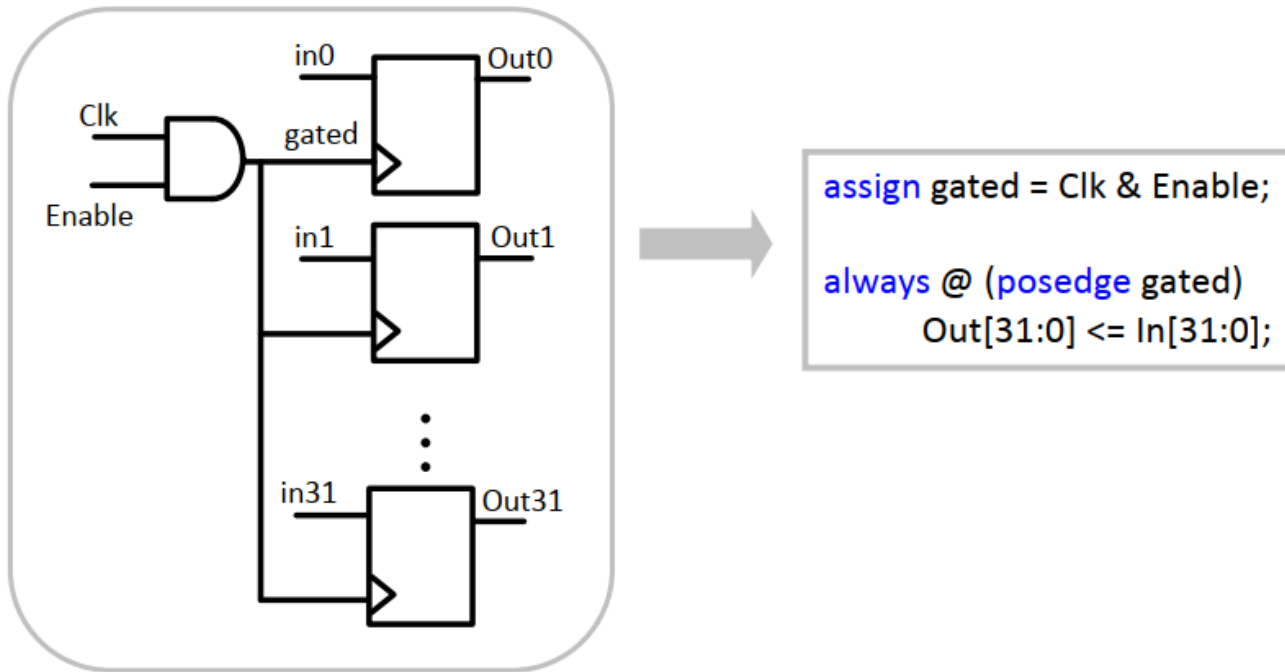
# Clock (No Gating)


- ❑ If clock gating is used avoid large fan-outs



- ❑ Large fan-out (deriving 32 flip flops)
- ❑ Large delay  $\Rightarrow$  high clock skew

## Clock (No Gating)

❑ Low Fan-out Alternative:

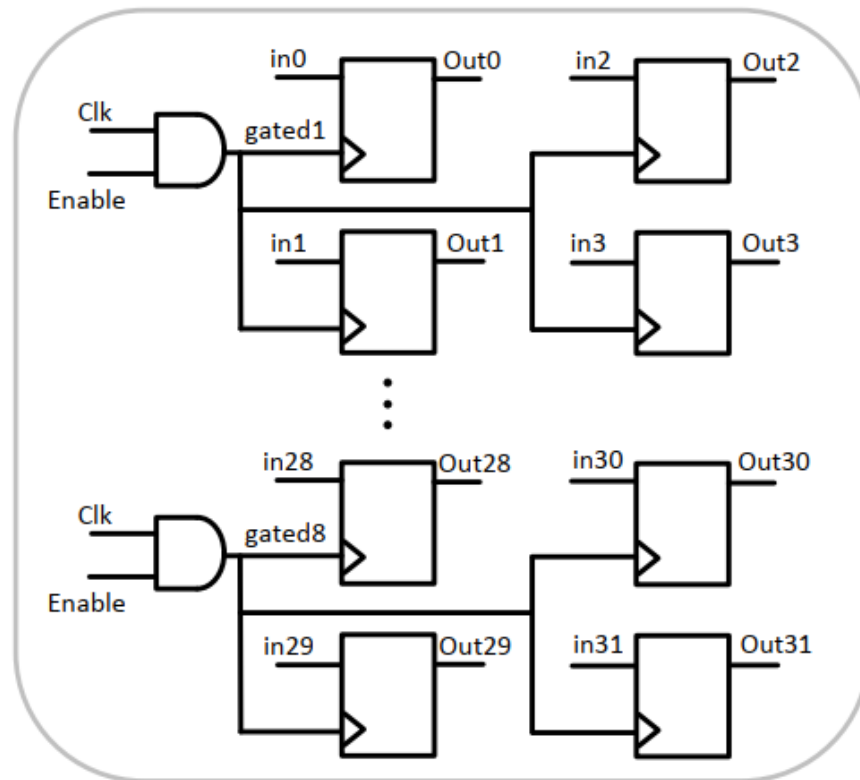

## Explicit “and” instantiation

```

and U1 (gated1, Clk, Enable);
and U2 (gated2, Clk, Enable);
  ⋮
and U8 (gated8, Clk, Enable);


always @ (posedge gated1)
    Out[3:0] <= In[3:0];
always @ (posedge gated2)
    Out[7:4] <= In[7:4];
  ⋮
always @ (posedge gated8)
    Out[31:28] <= In[31:28];

```


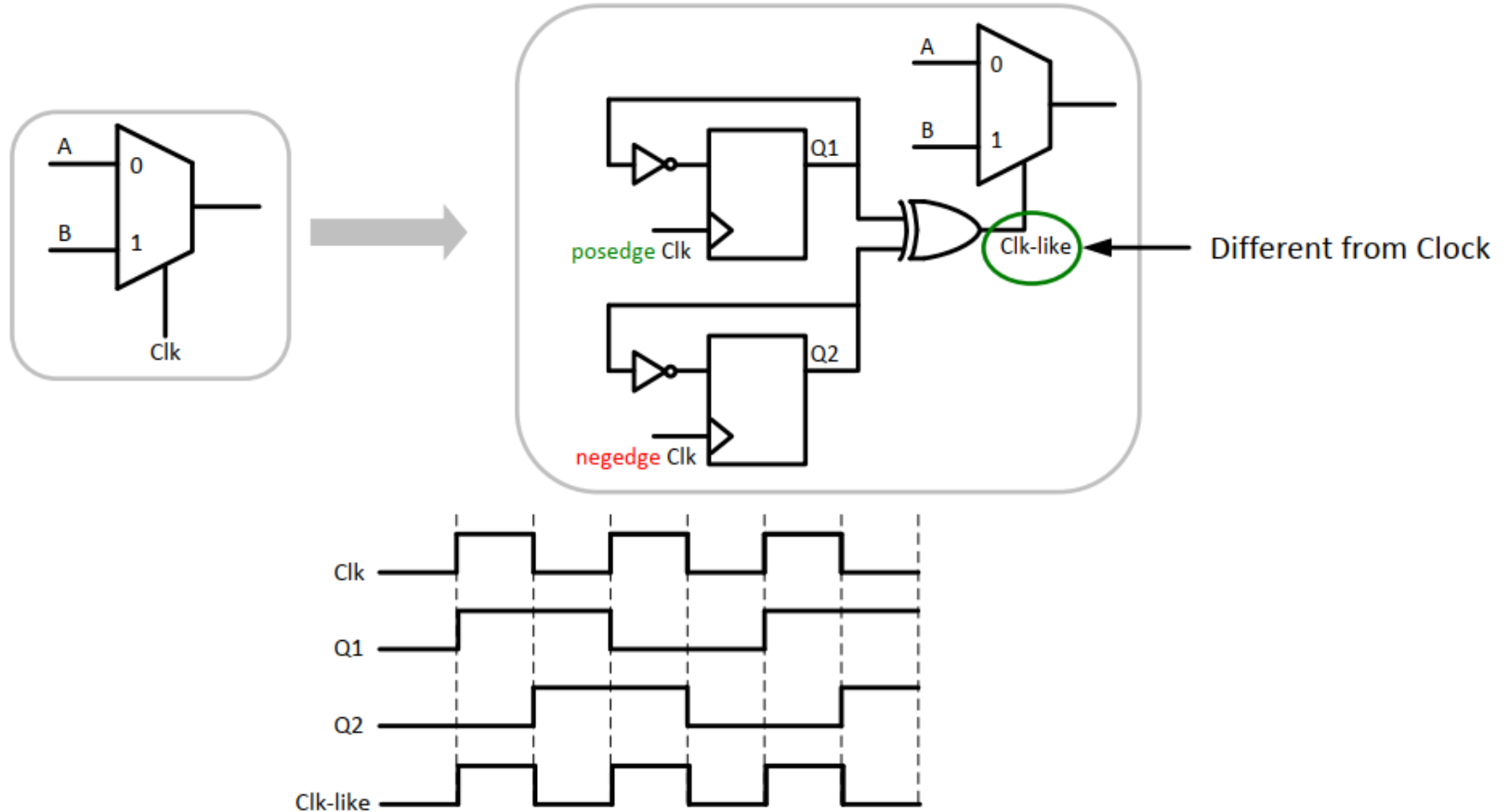
# Clock

- ❑ Do not use clock as an input or selector (results in an inefficient clock tree)




# Architectural Techniques : Critical Path

❑ Critical path in any design is the longest path between

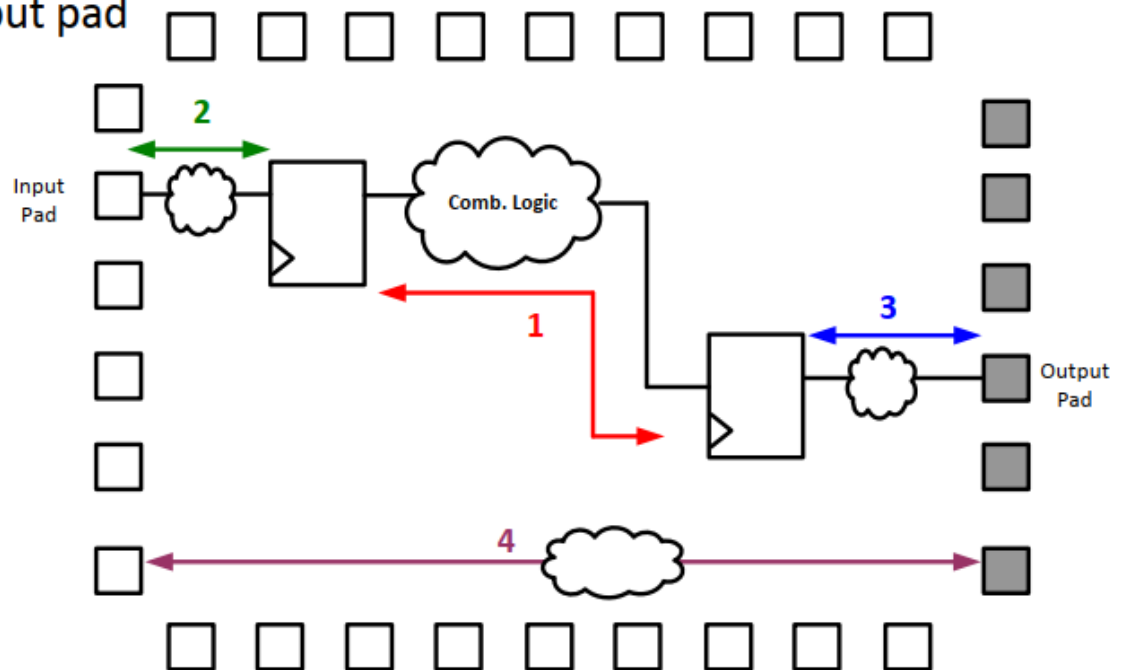1. Any two internal latches/flip-flops
2. An input pad and an internal latch
3. An internal latch and an output pad
4. An input pad and an output pad

Use FFs right after/before input/out pads to avoid the last three cases (off-chip and packaging delay)

The maximum delay between any two sequential elements in a design will determine the max clock speed



# Digital Design Metrics

□ Three primary physical characteristics of a digital design:

➤ **Speed**

- Throughput
- Latency
- Timing

➤ **Area**

➤ **Power**

# Digital Design Metrics

## ❑ Speed

### ➤ Throughput :

- The amount of data that is processed per clock cycle (bits per second)

### ➤ Latency

- The time between data input and processed data output (clock cycle)

### ➤ Timing

- The logic delays between sequential elements (clock period)
- When a design does not meet the timing it means the delay of the critical path is greater than the target clock period

# Maximum Clock Frequency: Critical Path

□ Maximum Clock Frequency:


$$F_{\max} = \frac{1}{T_{\text{clk-q}} + T_{\text{logic}} + T_{\text{setup}} + T_{\text{routing}} - T_{\text{skew}}}$$

- $T_{\text{clk-q}}$  : time from clock arrival until data arrives at Q
- $T_{\text{logic}}$  : propagation delay through logic between flip-flops
- $T_{\text{routing}}$  : routing delay between flip-flops
- $T_{\text{setup}}$  : minimum time data must arrive at D before the next rising edge of clock
- $T_{\text{skew}}$  : propagation delay of clock between the launch flip-flop and the capture flip-flop.

# Pipelining (to Improve Throughput)
 
## ❑ Pipelining:

- Comes from the idea of a water pipe: continue sending water without waiting the water in the pipe to be out
- Used to reduce the critical path of the design



## ❑ Advantageous:

- Reduction in the critical path
- Higher throughput (number of computed results in a give time)
- Increases the clock speed (or sampling speed)
- Reduces the power consumption at same speed

# Architectural Techniques :Pipelining

## ❑ Pipelining:

- Very similar to the assembly line in the auto industry
- The beauty of a pipelined design is that new data can begin processing before the prior data has finished, much like cars are processed on an assembly line.

